


# Cascaded DC-DC Converter Systems: Stability Criteria and Solutions

*Presented by*  
Xinbo Ruan

Center for More-Electric-Aircraft Power System  
Nanjing University of Aeronautics and Astronautics

- **Backgrounds**
- **General Impedance-Based Stability for Cascaded System**
- **Input Impedance Regulation for Load Converter**
- **Adaptive Impedance Adaptor**
- **Conclusions**

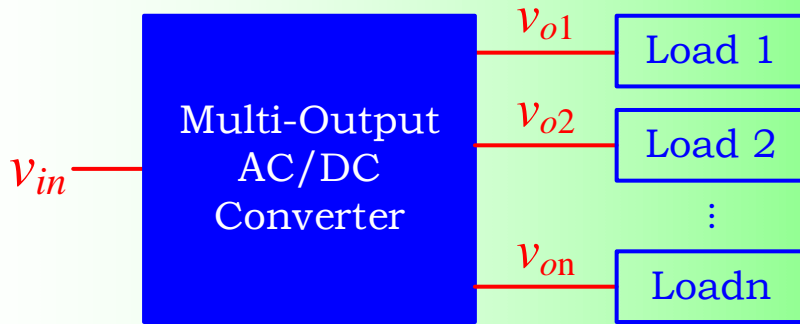- **Backgrounds**
- **General Impedance-Based Stability for Cascaded System**
- **Input Impedance Regulation for Load Converter**
- **Adaptive Impedance Adaptor**
- **Conclusions**




Centralized Power System

☹ Poor cross-regulation;

☹ Poor dynamic response;

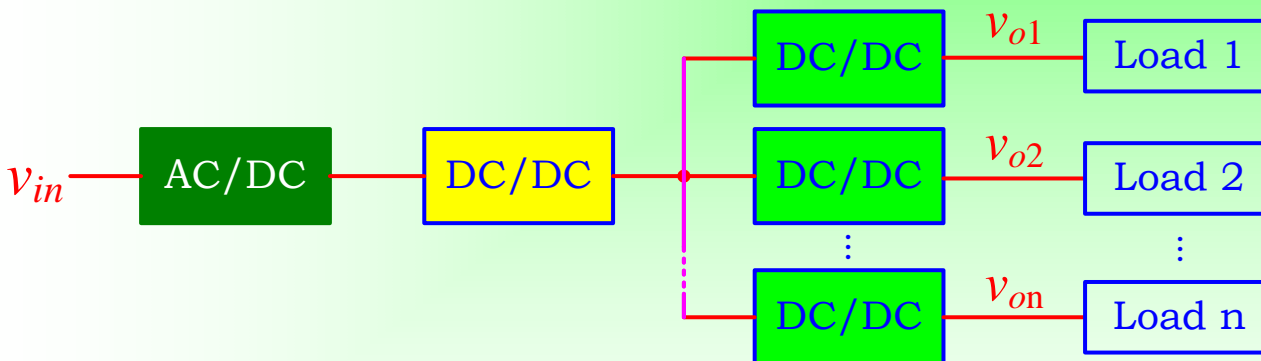☹ Large loss due to long distance between the power supply and load.



Distributed Power System

☺ Modular design;

☺ Tight regulation of each output.

☺ Lower loss in the transmission line.

## More-Electric- and All-Electric Aircrafts



## Aerospace Stations



## Warships



## Personal Computer




## Electric Vehicle



## Server



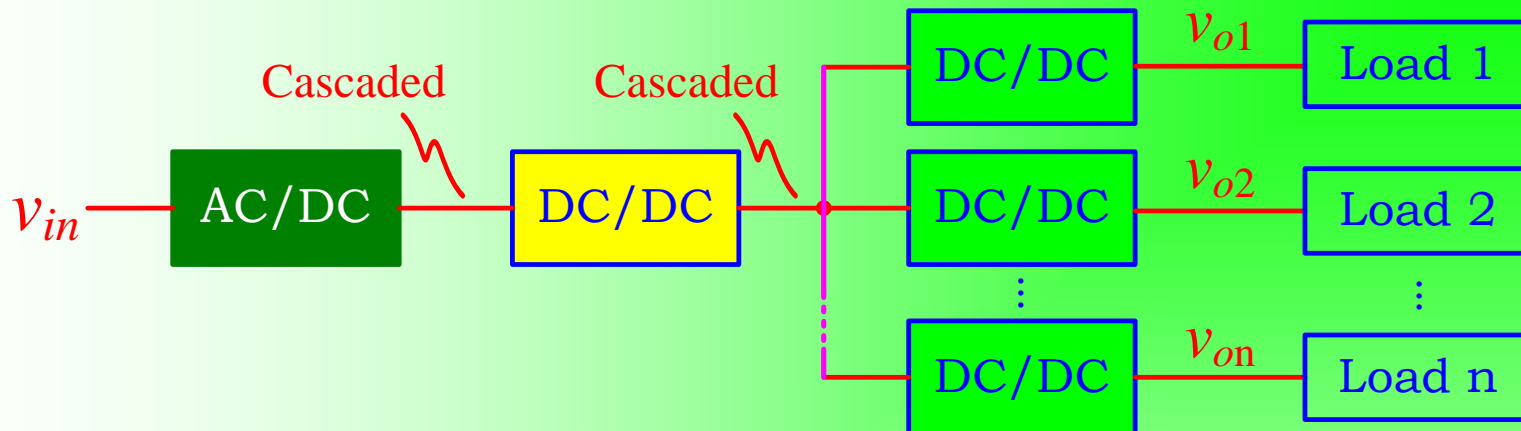


A Typical Distributed Power System

System stability  
criterion?

Solutions to  
improve  
system stability?

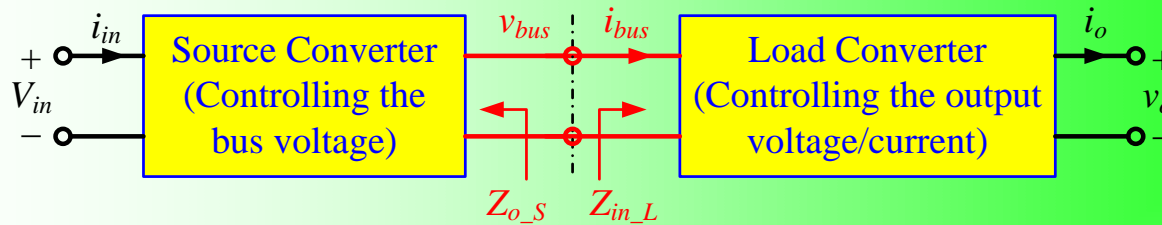
- Backgrounds
- **General Impedance-Based Stability for Cascaded System**
- Input Impedance Regulation for Load Converter
- Adaptive Impedance Adaptor
- Conclusions



Equivalent loop gain:

$$T_m = \frac{Z_{o\_S}(s)}{Z_{in\_L}(s)}$$

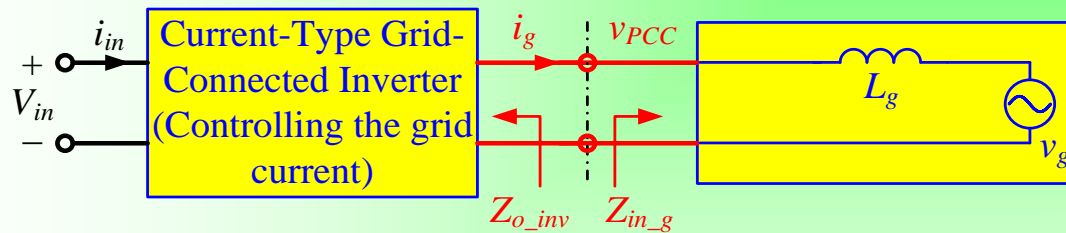R. D. Middlebrook, "Input filter considerations in design and application of switching regulators," in Proc. IEEE IAS, 1979.



Equivalent loop gain:


$$T_m = \frac{Z_{in\_g}(s)}{Z_{o\_inv}(s)}$$

J. Sun, "Impedance-based stability criterion for grid-connected inverters," IEEE Trans on. Power Electronics, vol. 26, no. 11, 2011.




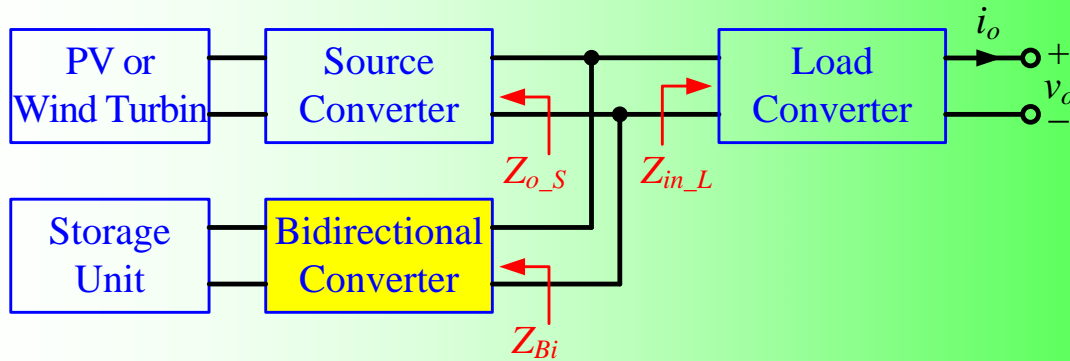The above two stability criteria is **contradictory**.







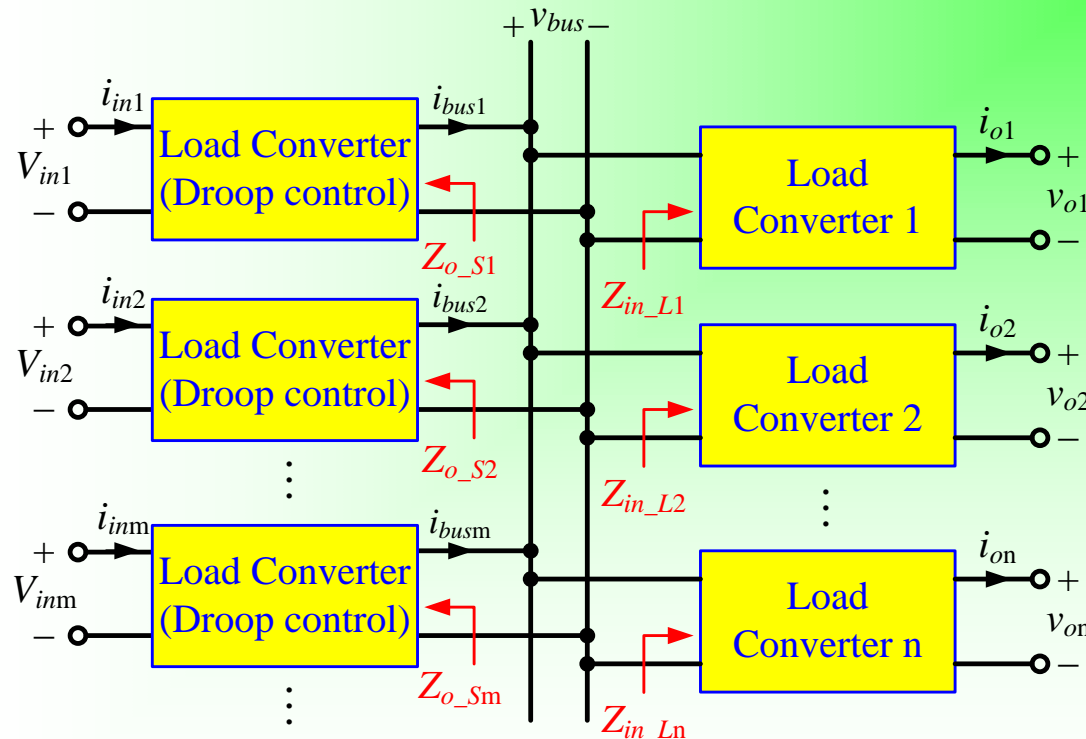
The bidirectional converter is a **source converter** or a **load converter**?



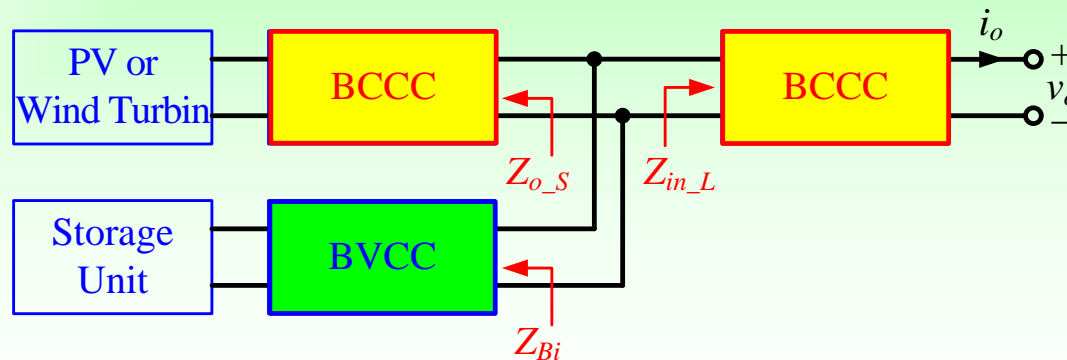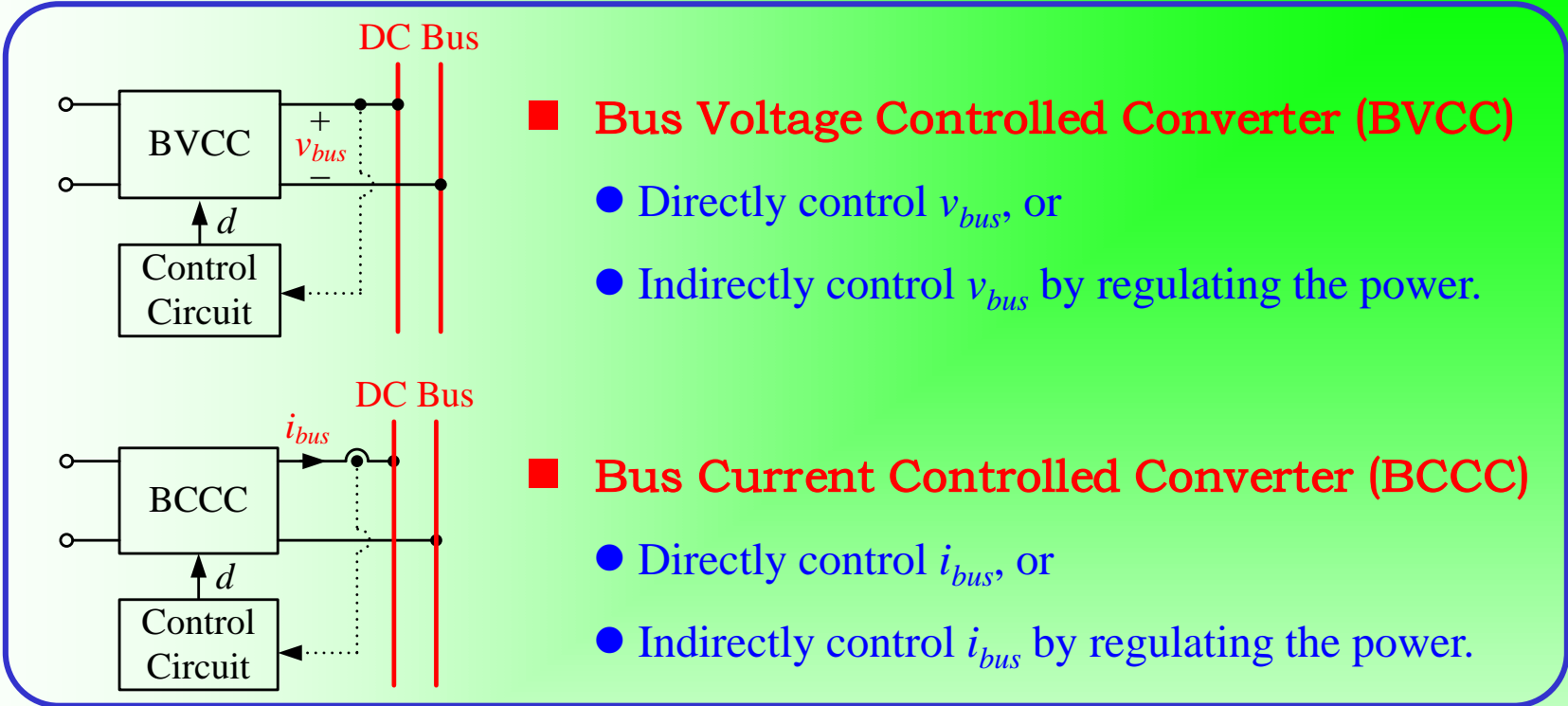
All the source converters control the intermediate bus voltage. How to obtain the **output impedance**?





## Standard Form of Cascaded System

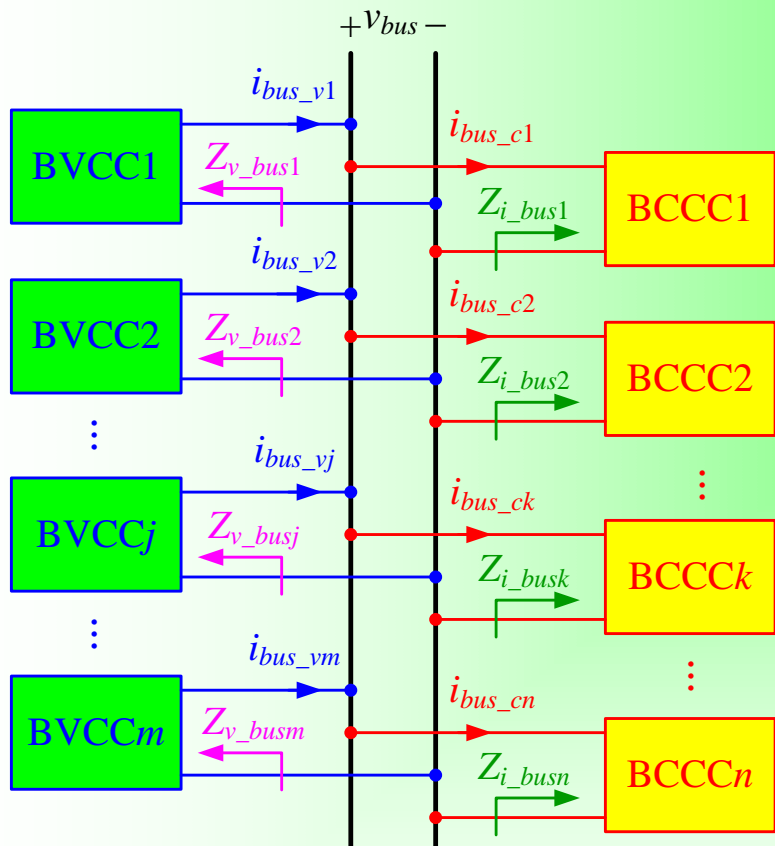


## Small-Signal Two-Port Model

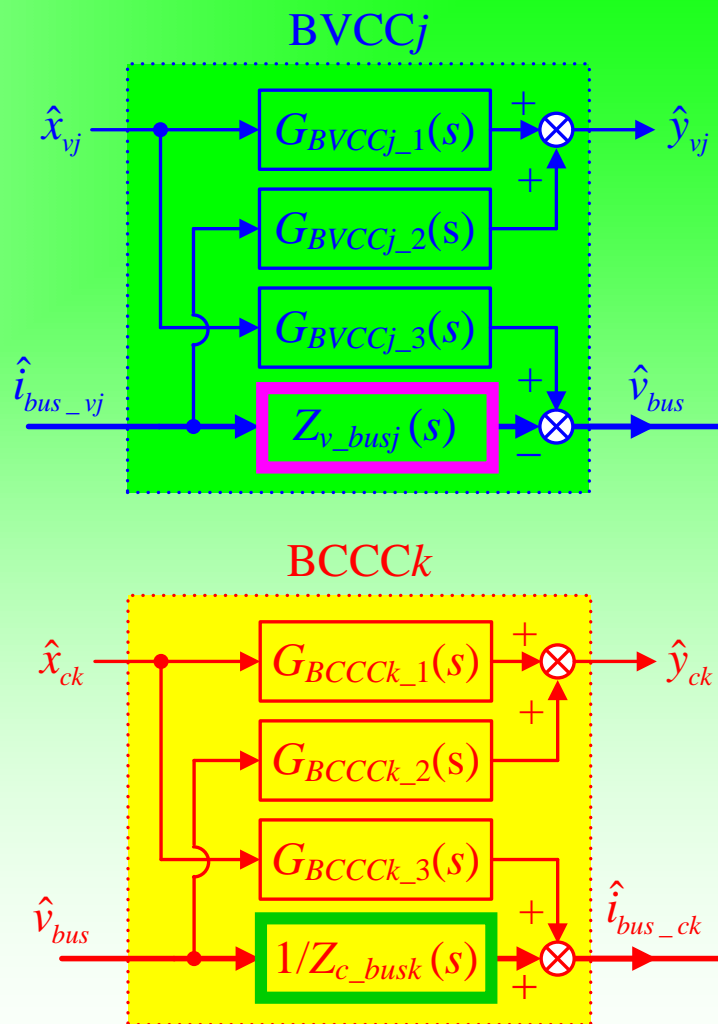

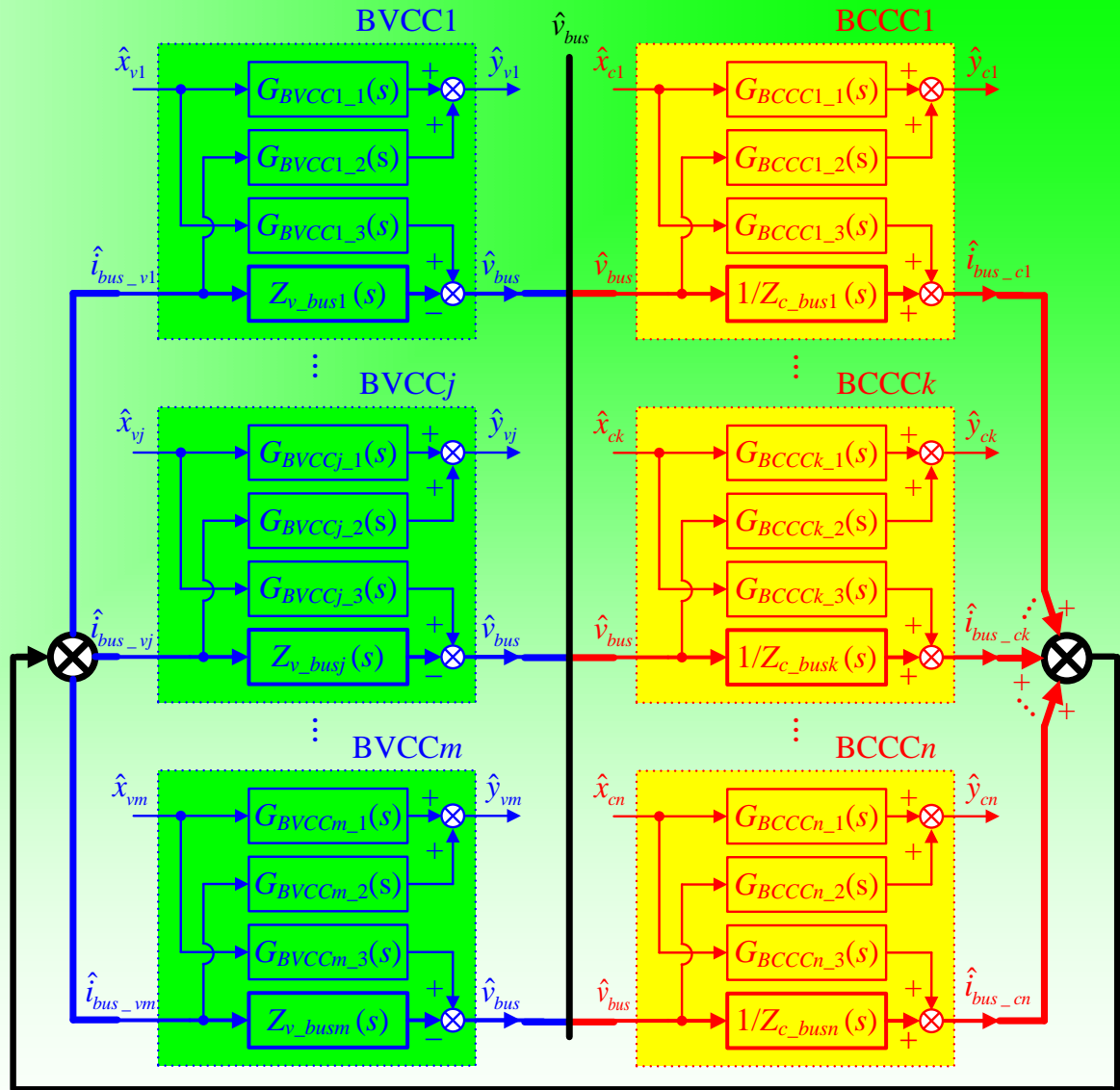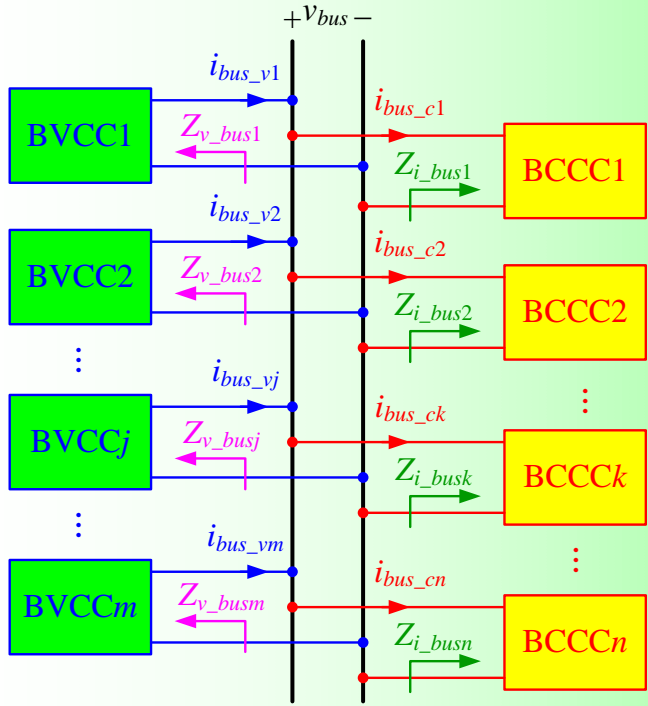

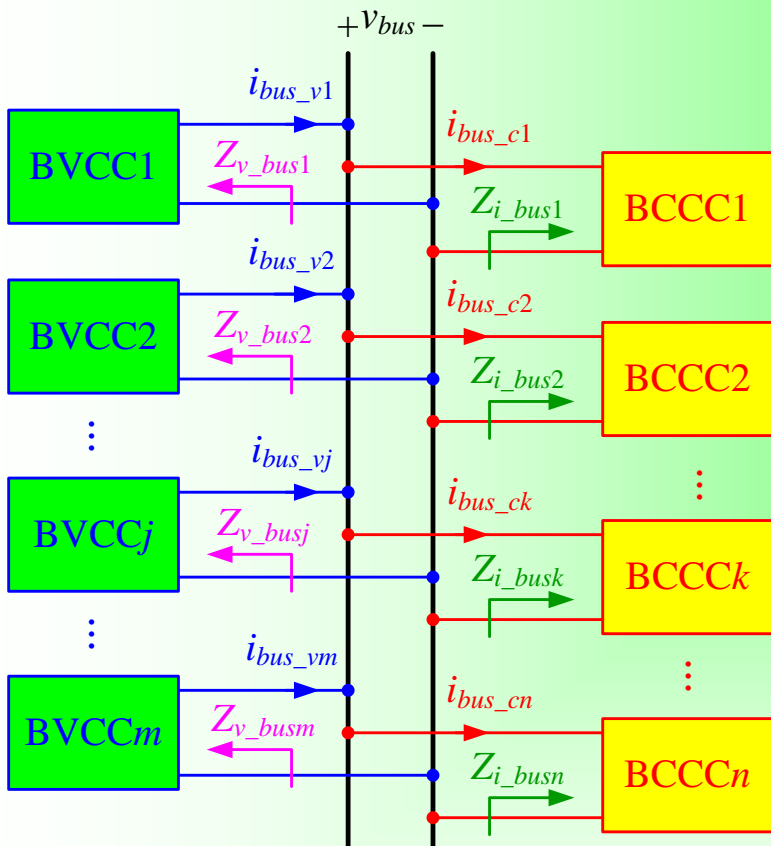**Equivalent Loop Gain of Cascaded System**

$$T_m = \frac{\left( \sum_{j=1}^m \frac{1}{Z_{v\_busj}} \right)^{-1}}{\left( \sum_{k=1}^n \frac{1}{Z_{i\_busk}} \right)^{-1}}$$



## Equivalent Loop Gain of Cascaded System

$$T_m = \frac{\left( \sum_{j=1}^m \frac{1}{Z_{v\_busj}} \right)^{-1}}{\left( \sum_{k=1}^n \frac{1}{Z_{i\_busk}} \right)^{-1}} = \frac{Z_{v\_bus}}{Z_{i\_bus}}$$

$Z_{v\_bus}$ : Shunt impedance of the **bus-side-port-impedances** of all the BVCCs.


$Z_{i\_bus}$ : Shunt impedance of the **bus-side-port-impedances** of all the BCCCs.

## General Impedance-Based Stability Criterion of Cascaded System


- Each converter is stable when working alone;
- $T_m$  satisfies the Nyquist criterion.
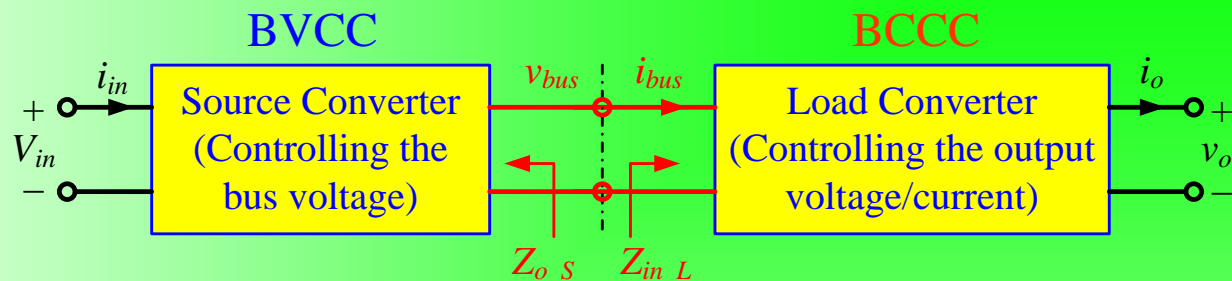
## Equivalent Loop Gain

$$T_m = \frac{\left( \sum_{j=1}^m \frac{1}{Z_{v\_busj}} \right)^{-1}}{\left( \sum_{k=1}^n \frac{1}{Z_{i\_busk}} \right)^{-1}}$$



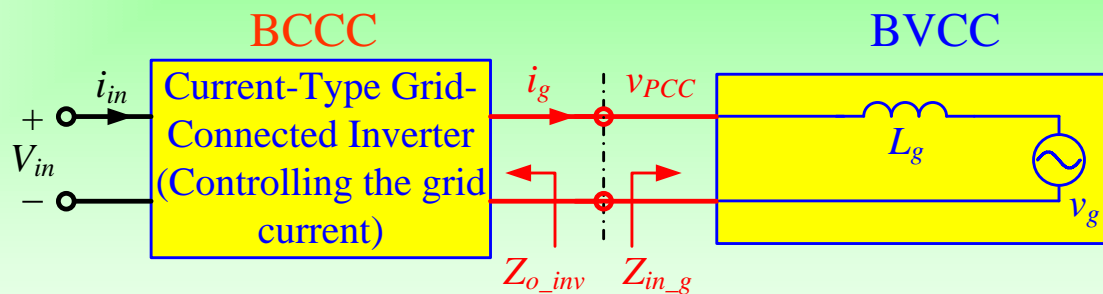
Equivalent loop gain:  $T_m = \frac{Z_{o\_S}(s)}{Z_{in\_L}(s)}$



Equivalent loop gain:  $T_m = \frac{Z_{in\_g}(s)}{Z_{o\_inv}(s)}$
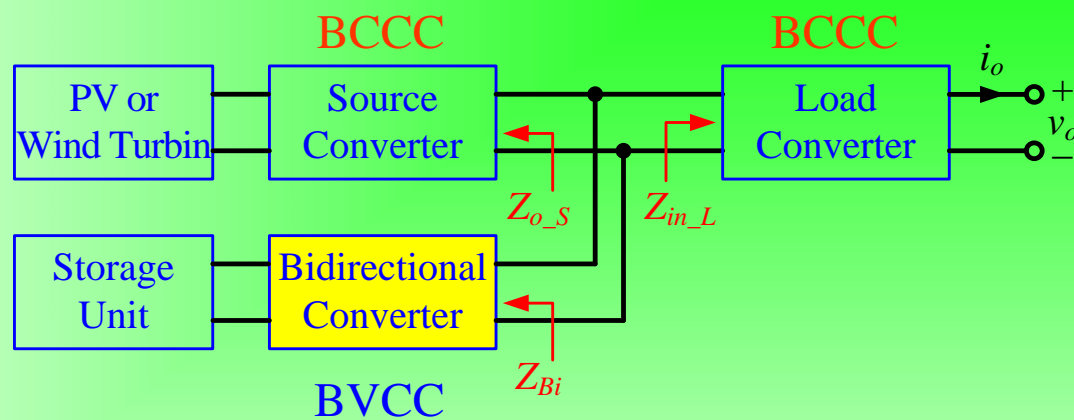
## Equivalent Loop Gain


$$T_m = \frac{\left( \sum_{j=1}^m \frac{1}{Z_{v\_busj}} \right)^{-1}}{\left( \sum_{k=1}^n \frac{1}{Z_{i\_busk}} \right)^{-1}}$$



Equivalent loop gain:  $T_m = \frac{Z_{Bi}(s)}{Z_{o\_s} // Z_{in\_L}(s)}$


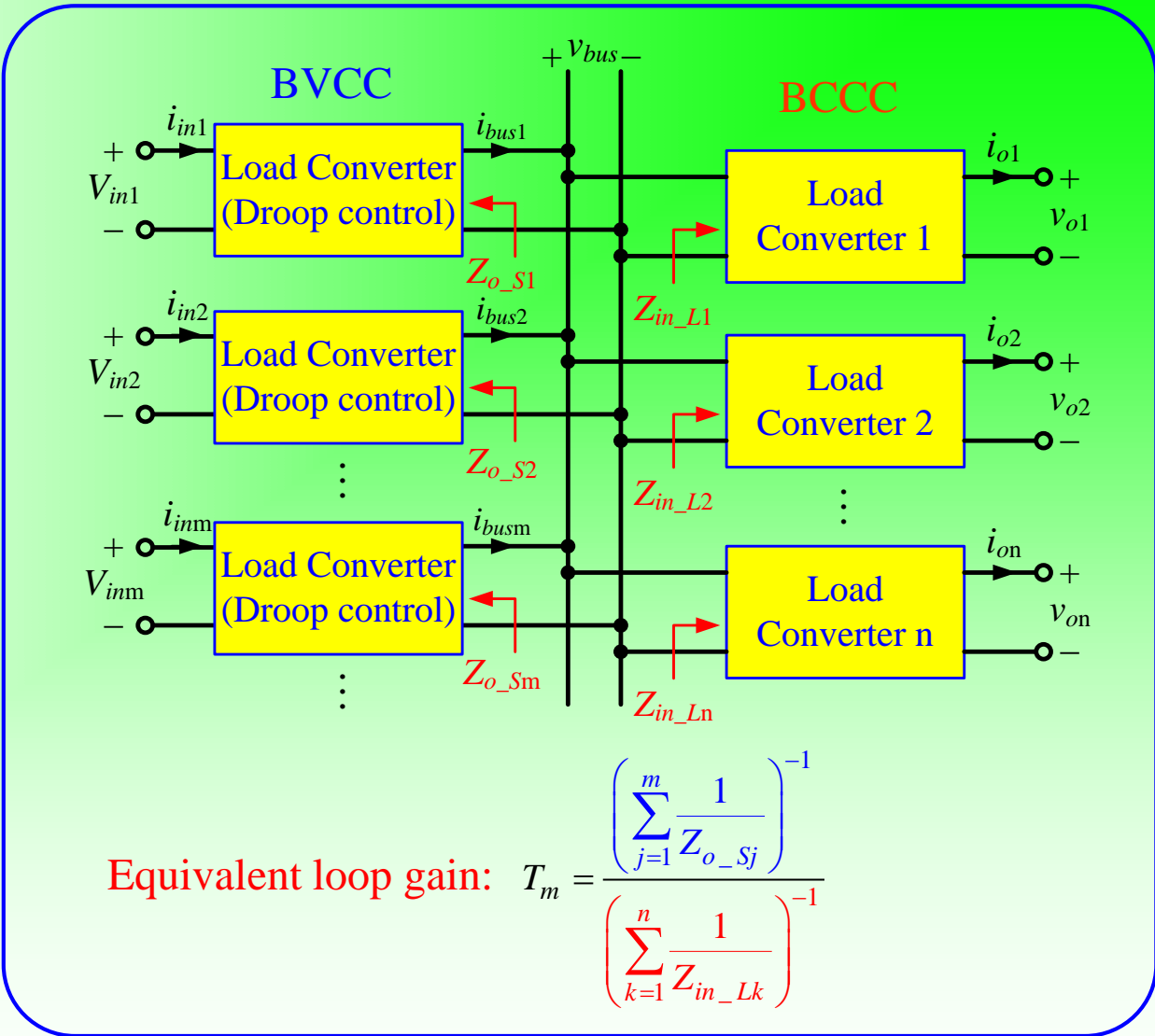
**Equivalent Loop Gain**

$$T_m = \frac{\left( \sum_{j=1}^m \frac{1}{Z_{v\_busj}} \right)^{-1}}{\left( \sum_{k=1}^n \frac{1}{Z_{i\_busk}} \right)^{-1}}$$





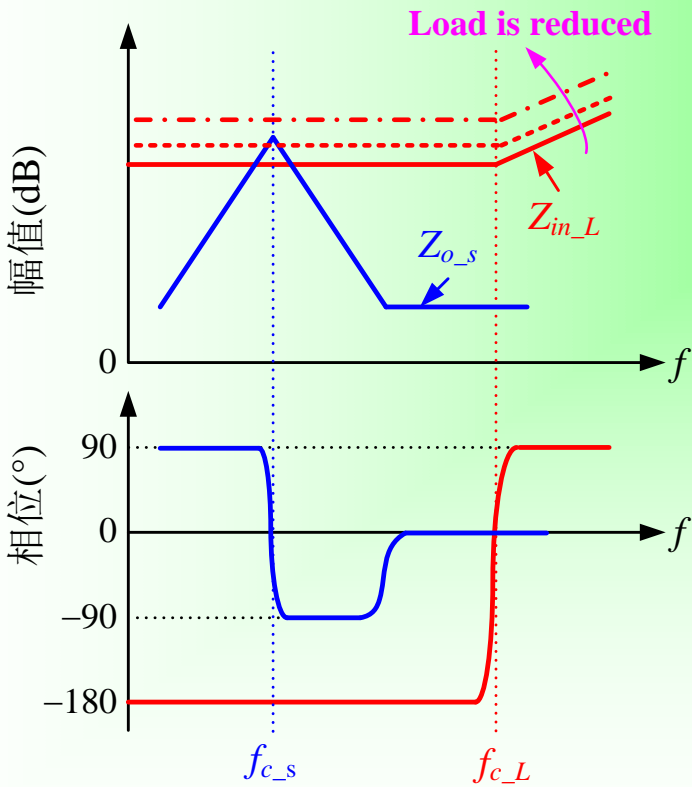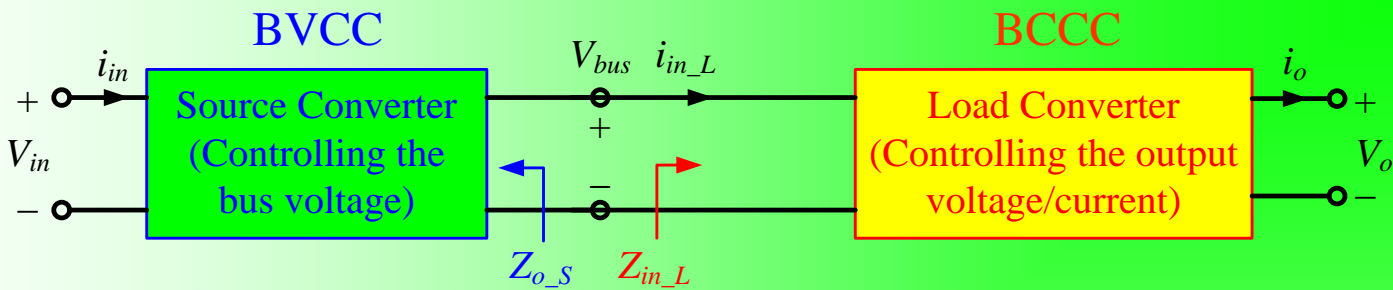- Backgrounds
- General Impedance-Based Stability for Cascaded System
- Input Impedance Regulation for Load Converter**
- Adaptive Impedance Adaptor
- Conclusions





### Load Converter

- $f < f_{c\_L}$ ,  $Z_{in\_L} = -V_{bus}^2 / P_o$  Negative resistor
- $f > f_{c\_L}$ ,  $Z_{in\_L}$  behaves as an inductor.
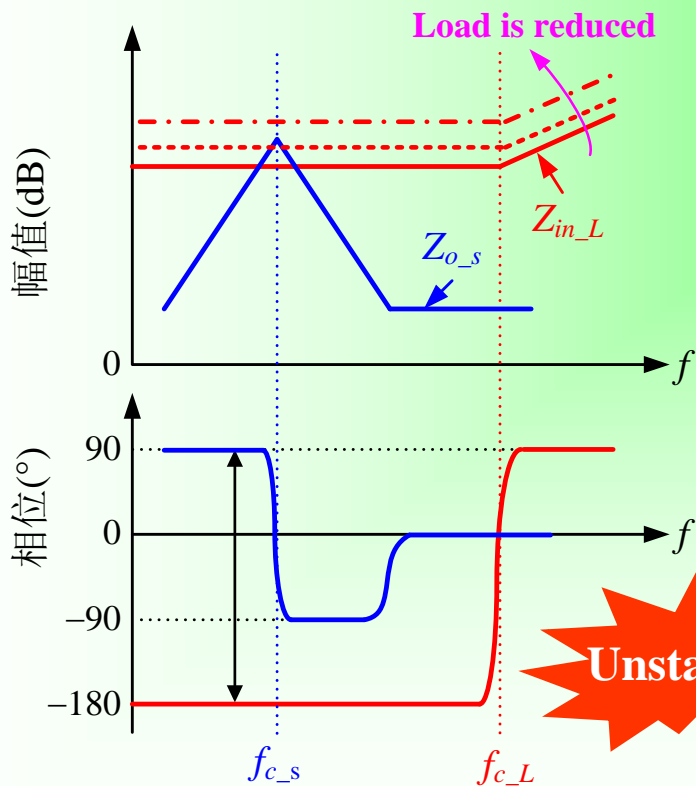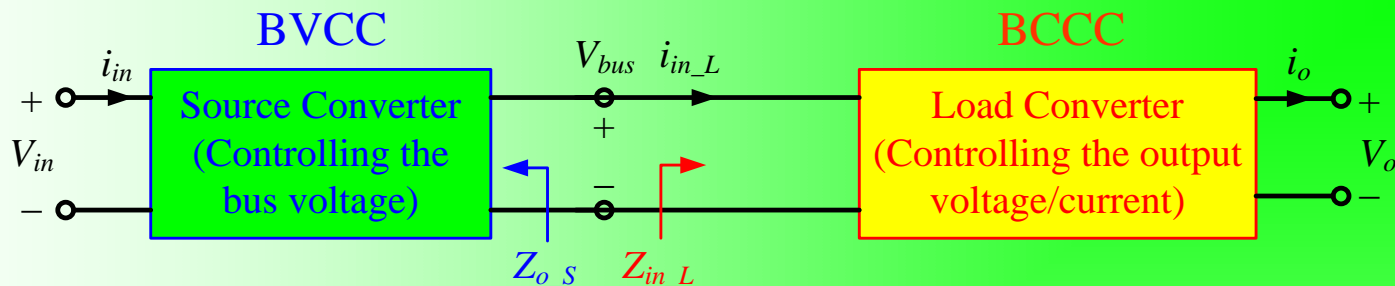
### Source Converter


- At the cut-off frequency  $f_{c\_S}$ ,  $Z_{o\_S}$  has a resonant peak.
- The magnitude of the resonant peak is **inversely proportional to the output filter capacitor.**




Equivalent loop gain: 
$$T_m = \frac{Z_{o\_S}(s)}{Z_{in\_L}(s)}$$

$T_m$  satisfied Nyquist criterion

- In the entire frequency range,  $Z_{o\_S}$  never intersects with  $Z_{in\_L}$ , i.e.,  $|Z_{o\_S}| < |Z_{in\_L}|$ ; or
- At the frequency of intersection,  $\angle Z_{o\_S} - \angle Z_{in\_L} < 180^\circ$ .

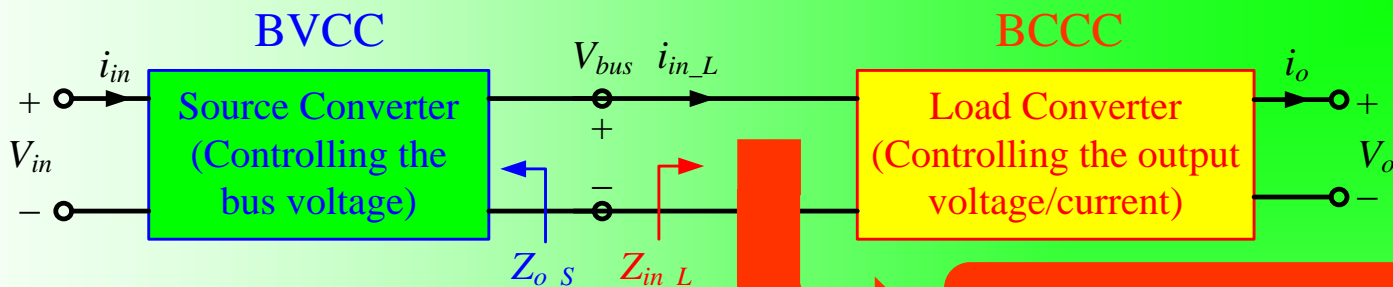


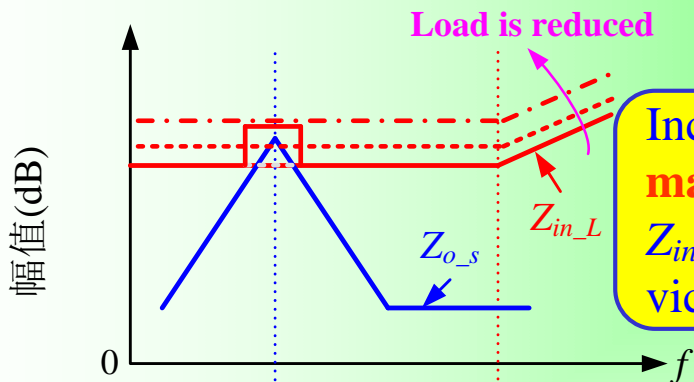Introduce a virtual impedance  $Z_{vir}$  at the bus-side of load converter



Increase the magnitude of  $Z_{in\_L}$  in the vicinity of  $f_{c\_S}$

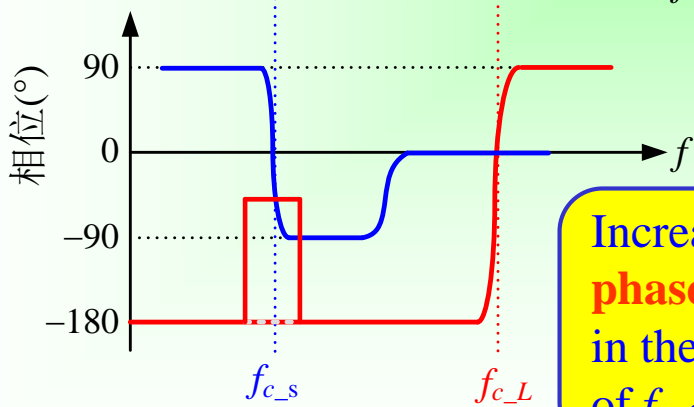
Equivalent loop gain: 
$$T_m = \frac{Z_{o\_S}(s)}{Z_{in\_L}(s)}$$




Increase the phase of  $Z_{in\_L}$  in the vicinity of  $f_{c\_S}$

$T_m$  satisfied Nyquist criterion



- In the entire frequency range,  $Z_{o\_S}$  never intersects with  $Z_{in\_L}$ , i.e.,  $|Z_{o\_S}| < |Z_{in\_L}|$ ; or
- At the frequency of intersection,  $\angle Z_{o\_S} - \angle Z_{in\_L} < 180^\circ$ .


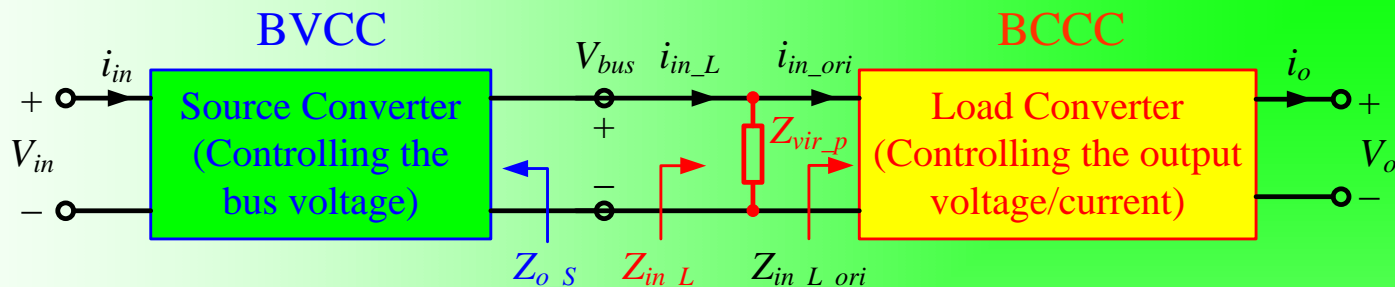




Parallel Virtual Impedance (PVI)

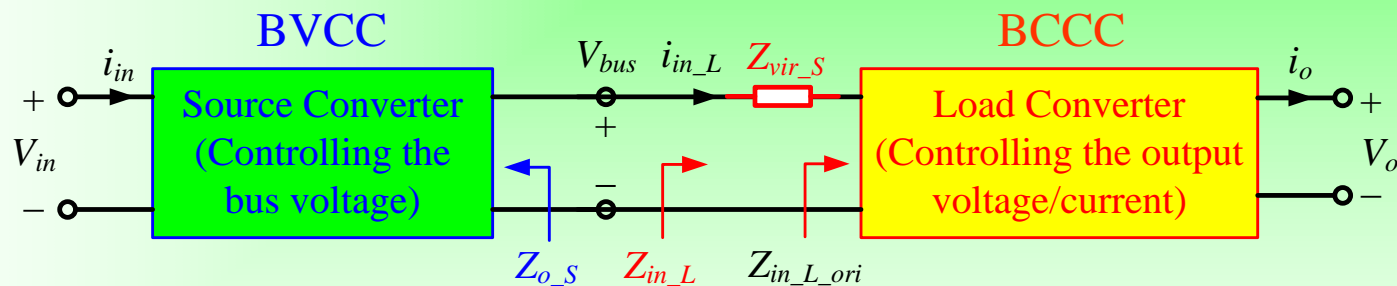

Series Virtual Impedance (SVI)

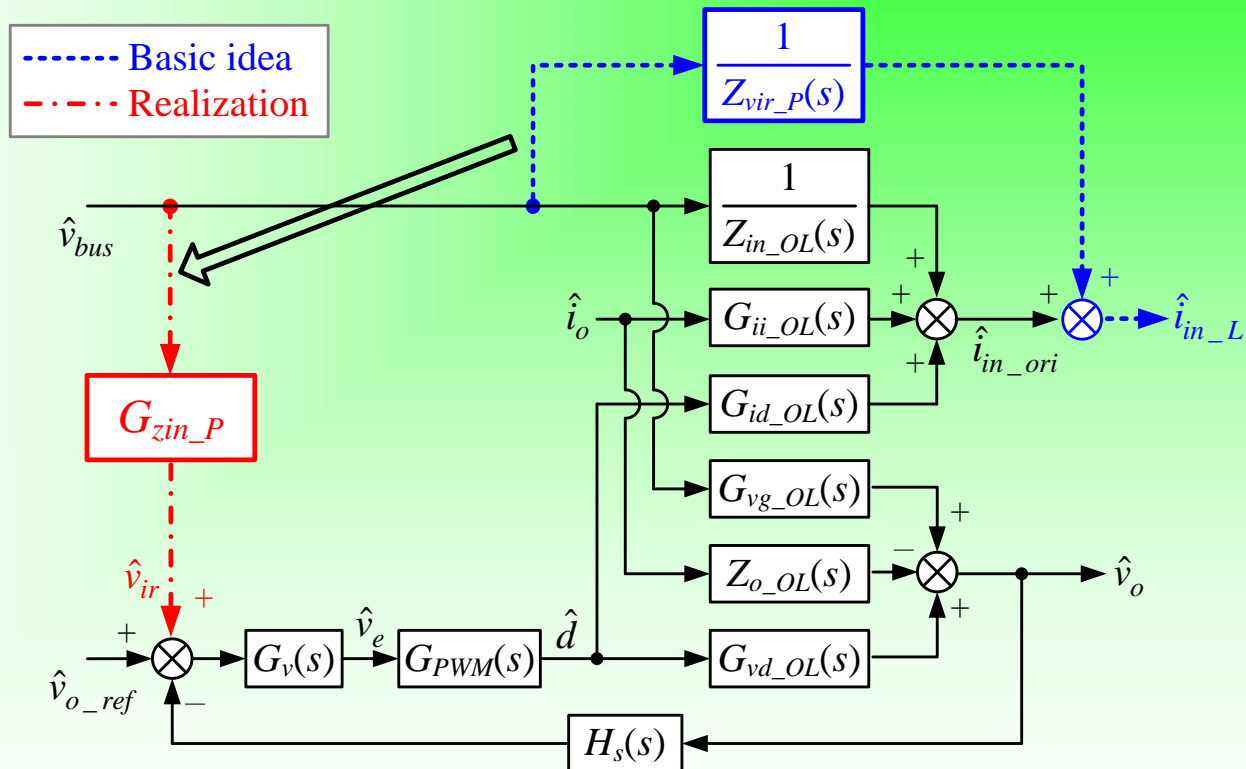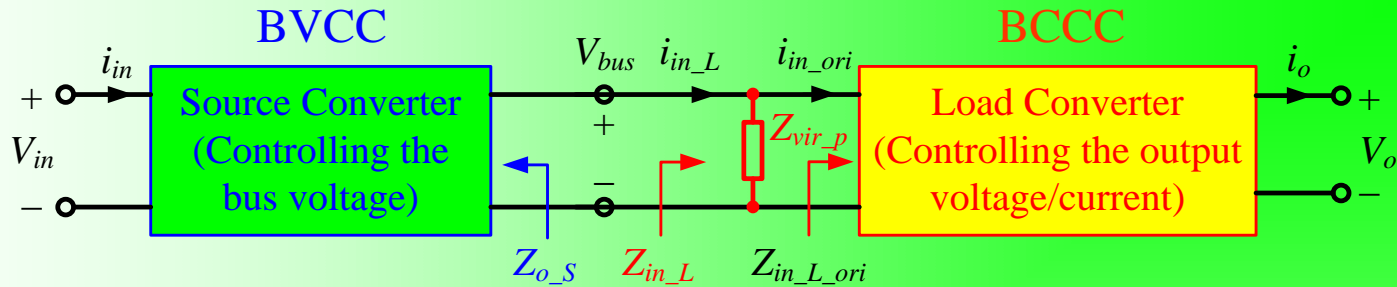

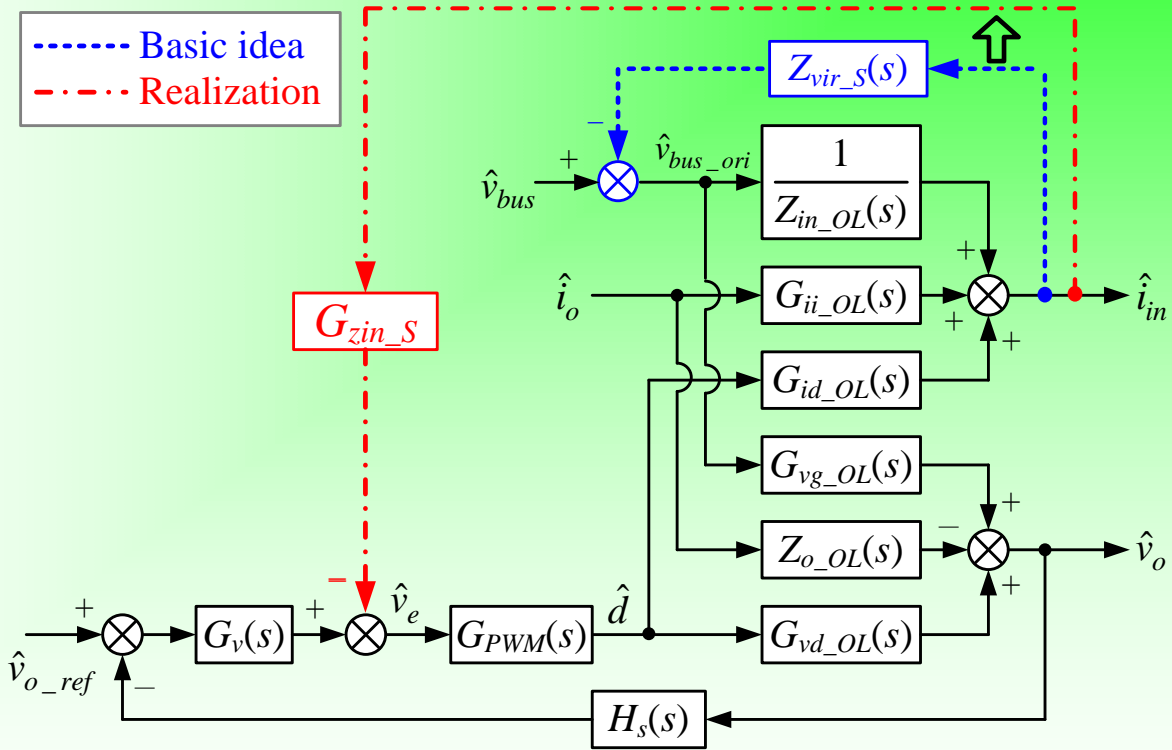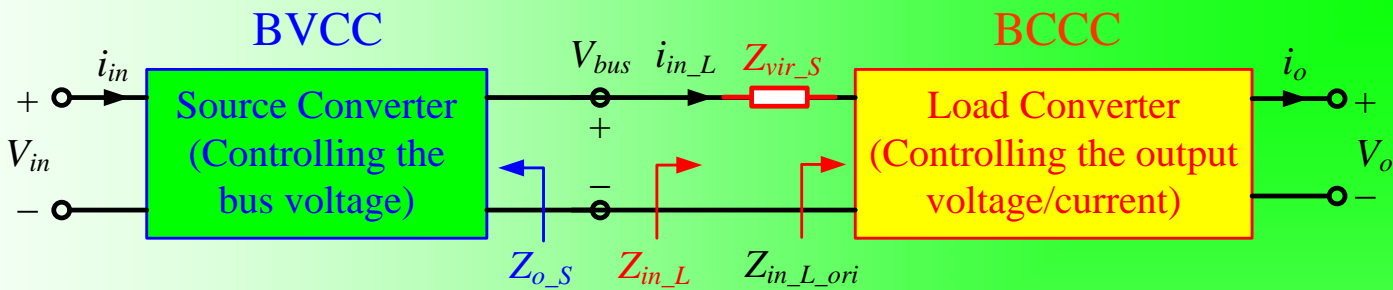

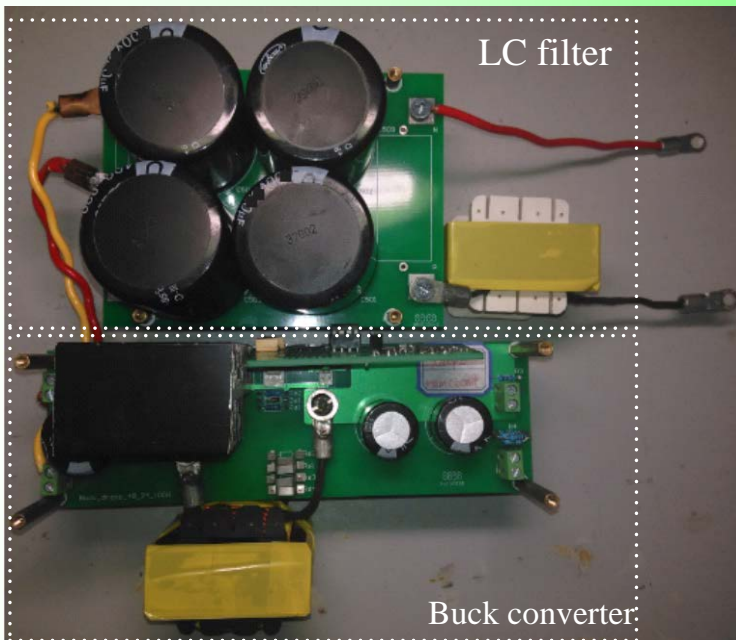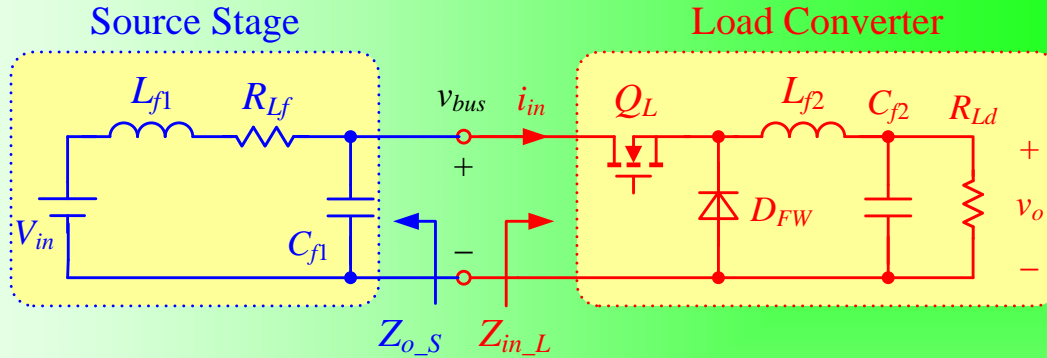


- Input voltage  $V_{in}$ : 48 VDC
- Output voltage  $V_o$ : 12 VDC
- Rated output power  $P_o$ : 100 W


- Input filter inductor  $L_{f1}$ : 700  $\mu$ H
- Input filter capacitor  $C_{f1}$ : 68  $\mu$ F

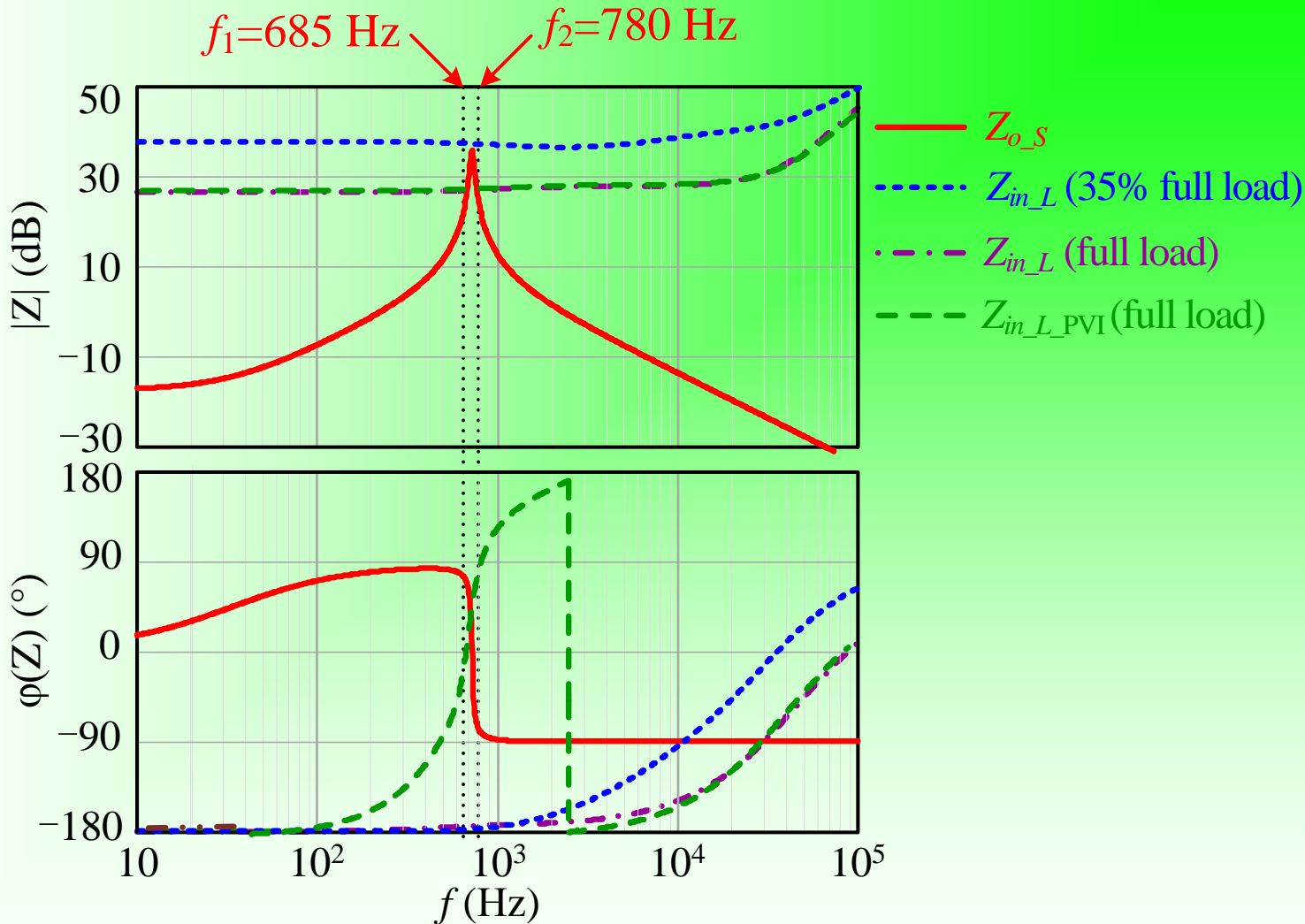- Output filter inductor  $L_{f2}$ : 33  $\mu$ H
- Output filter capacitor  $C_{f2}$ : 2400  $\mu$ F
- Switching frequency  $f_s$ : 100 kHz






	W/O parallel virtual impedance	With parallel virtual impedance
Full Load	<p><math>i_o</math>: [5 A/div] <math>v_{bus}</math>: [5 V/div] <math>v_o</math>: [1 V/div] Time: [500 <math>\mu</math>s/div]</p>	<p><math>i_o</math>: [5 A/div] <math>v_{bus}</math>: [5 V/div] <math>v_o</math>: [1 V/div] Time: [500 <math>\mu</math>s/div]</p>
Half Load	<p><math>i_o</math>: [5 A/div] <math>v_{bus}</math>: [5 V/div] <math>v_o</math>: [1 V/div] Time: [500 <math>\mu</math>s/div]</p>	<p><math>i_o</math>: [5 A/div] <math>v_{bus}</math>: [5 V/div] <math>v_o</math>: [1 V/div] Time: [500 <math>\mu</math>s/div]</p>
35% Full Load	<p><math>i_o</math>: [5 A/div] <math>v_{bus}</math>: [5 V/div] <math>v_o</math>: [1 V/div] Time: [500 <math>\mu</math>s/div]</p>	<p><math>i_o</math>: [5 A/div] <math>v_{bus}</math>: [5 V/div] <math>v_o</math>: [1 V/div] Time: [500 <math>\mu</math>s/div]</p>


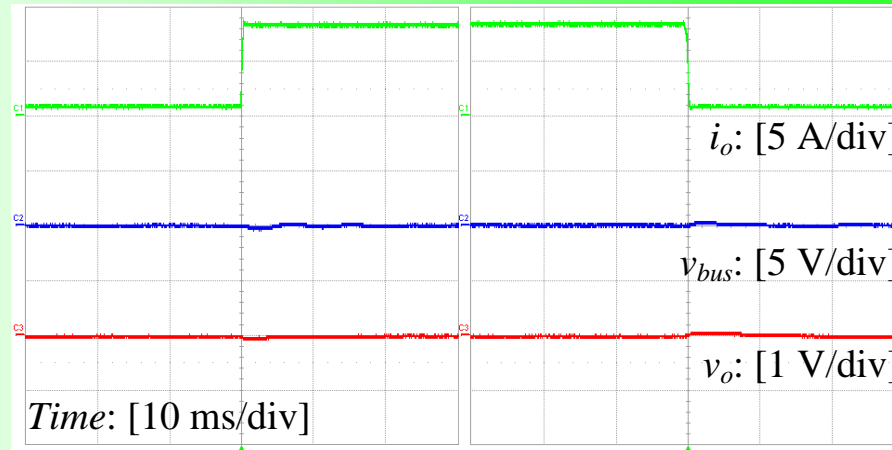


The load is stepped change

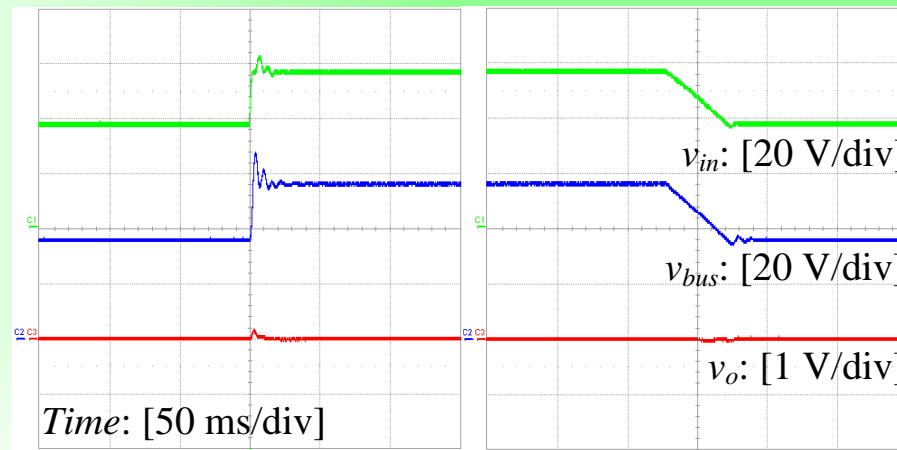

The input voltage is stepped changed

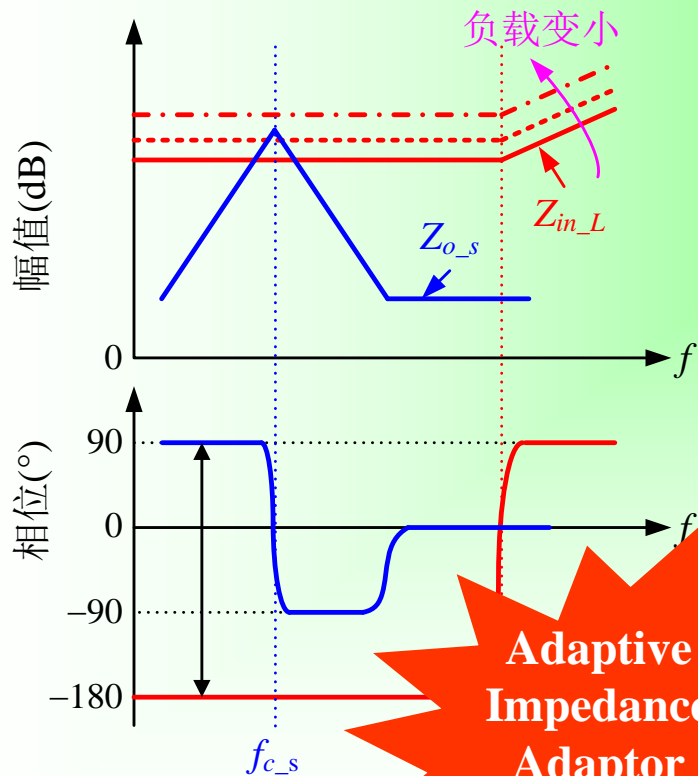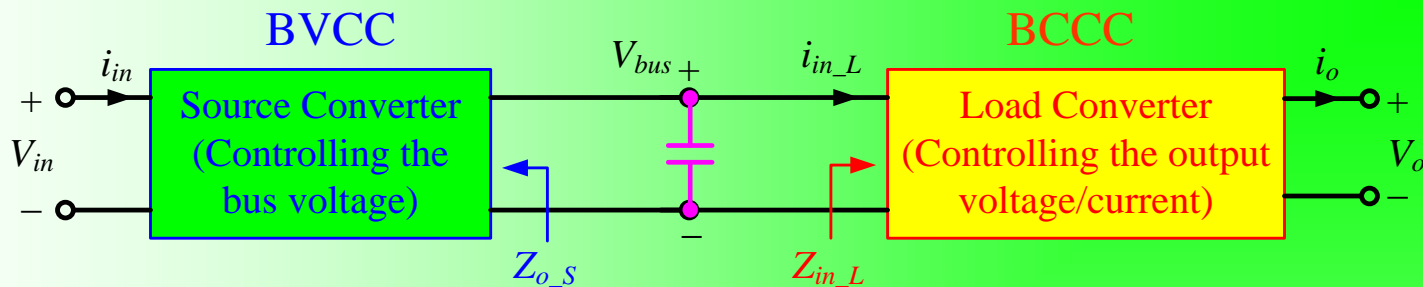- Backgrounds
- General Impedance-Based Stability for Cascaded System
- Input Impedance Regulation for Load Converter
- Adaptive Impedance Adaptor**
- Conclusions



Reduce **the magnitude** of the BVCC's bus-side port impedance, and it is **adaptively vary with the load**, ensuring the cascaded system stable **critically**.








Add a capacitor in parallel with the dc bus  
**The capacitance adaptively vary with the load.**



Propose an **active capacitor converter**, and the **emulated capacitor is required to vary with the load.**

**Adaptive  
Impedance  
Adaptor**

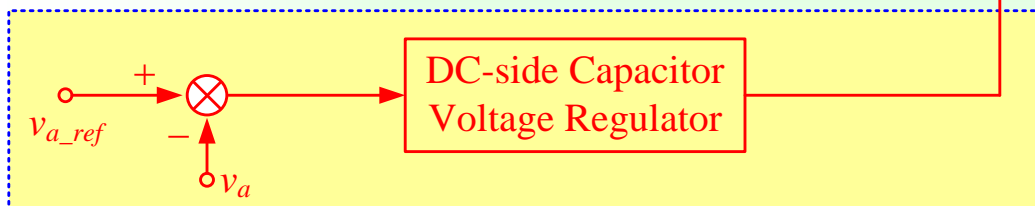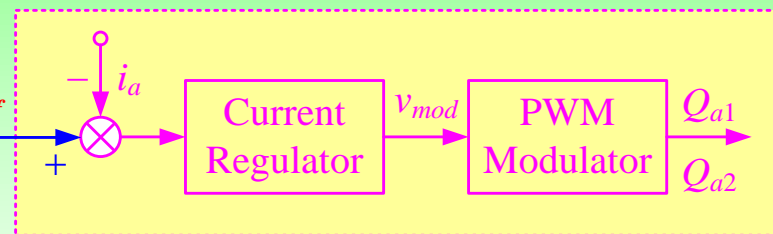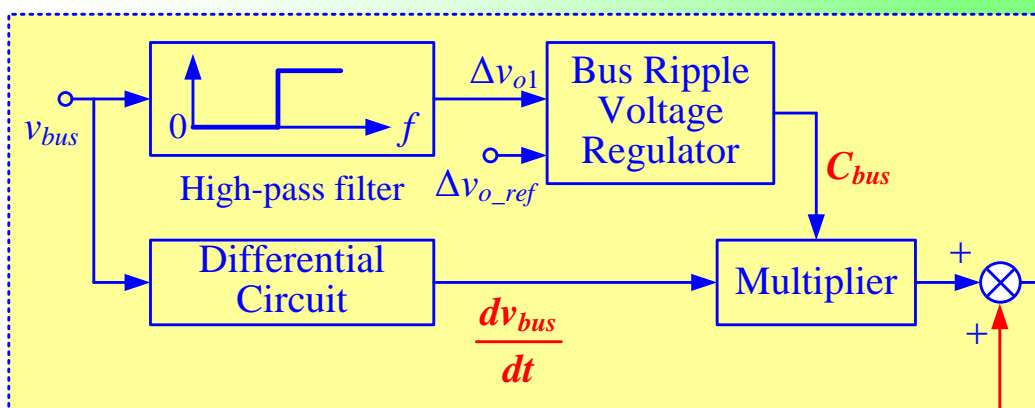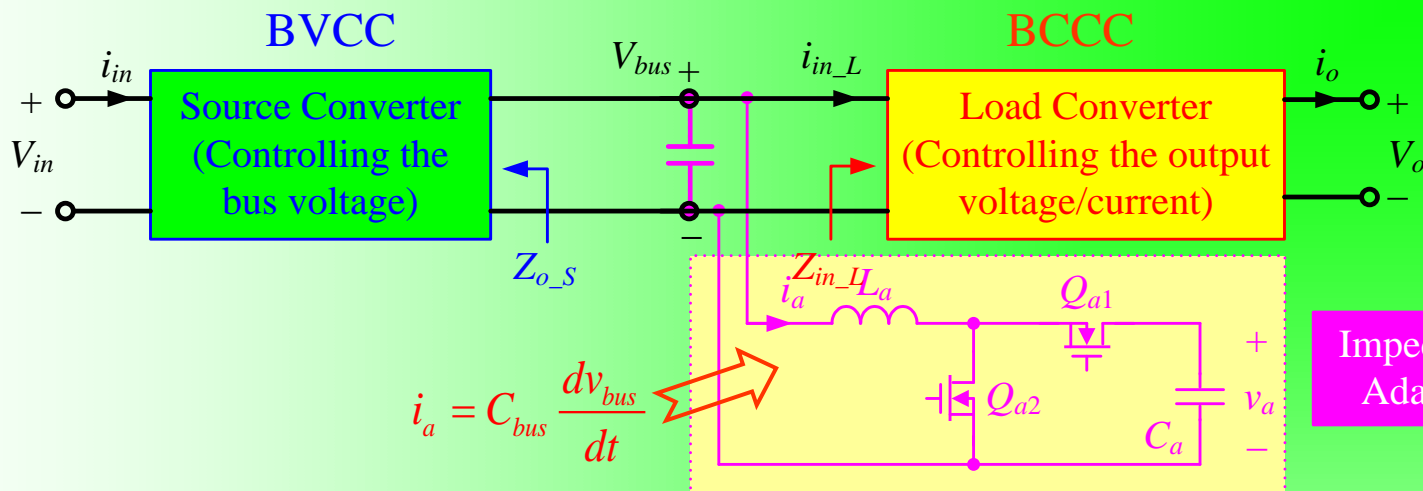

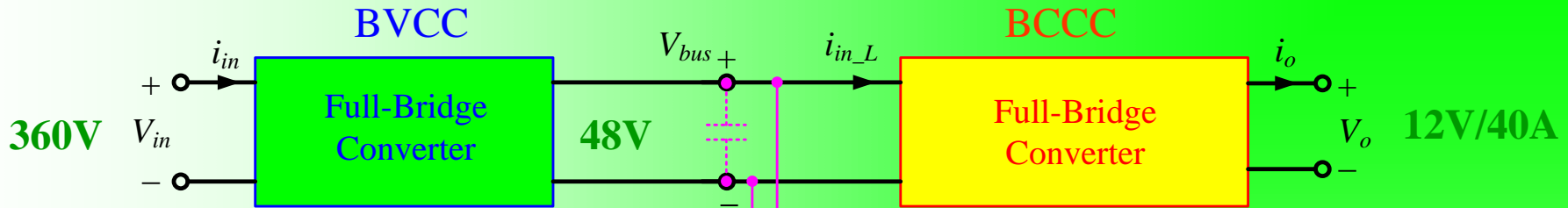

## Source Converter (Full-Bridge)



- Winding ratio of transformer: 5
- Filter inductor  $L_{f1}$ : 150  $\mu\text{H}$
- Filter capacitor  $C_{f1}$ : 680  $\mu\text{F}$


## Load Converter (Full-Bridge)

- Winding ratio of transformer: 3
- Filter inductor  $L_{f2}$ : 2.2  $\mu\text{H}$
- Filter capacitor  $C_{f2}$ : 4700  $\mu\text{F}$
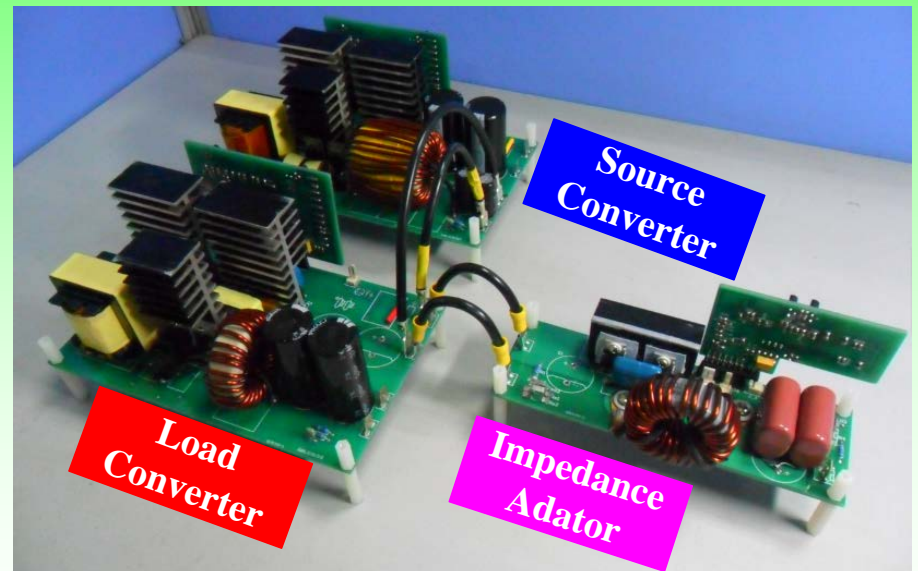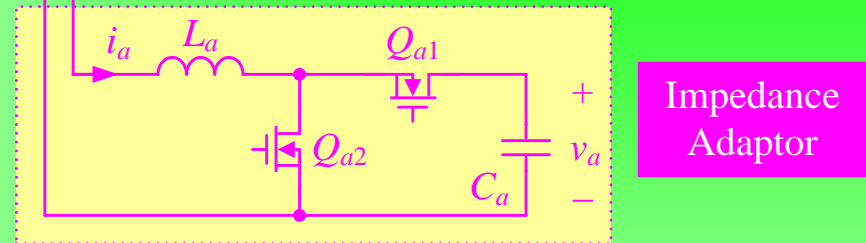
## Impedance Adaptor (Buck/Boost)






- Inductor  $L_a$ : 395  $\mu\text{H}$
- DC-side capacitor  $C_a$ : 20  $\mu\text{F}$




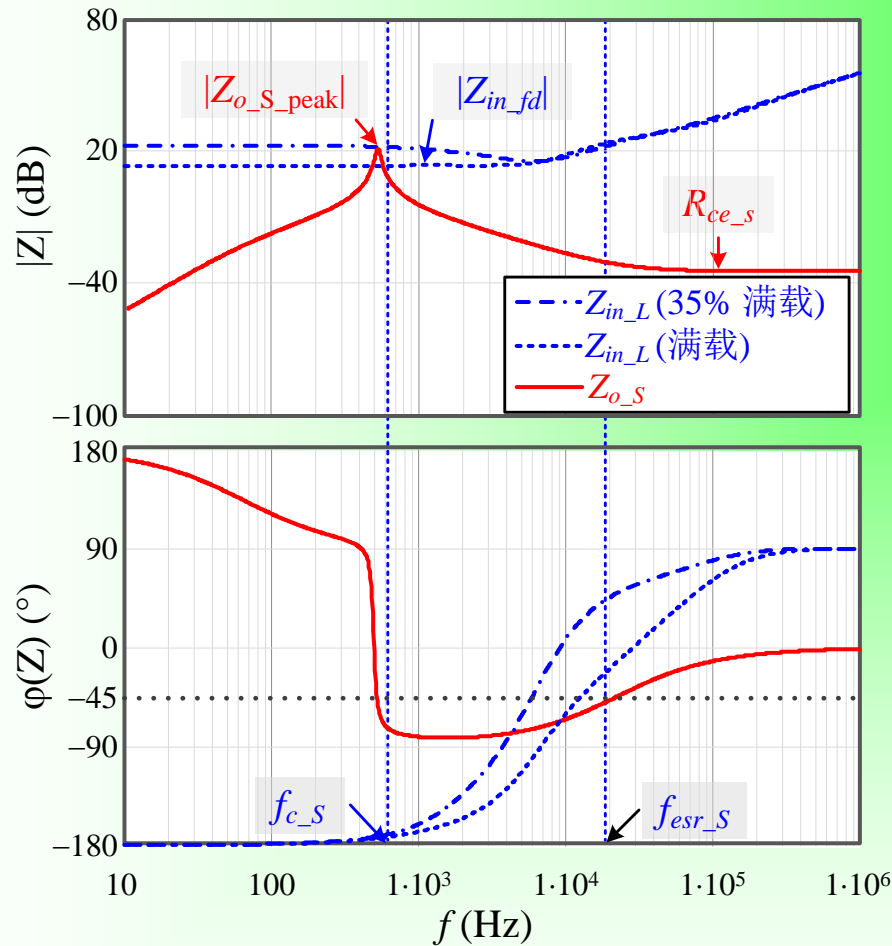

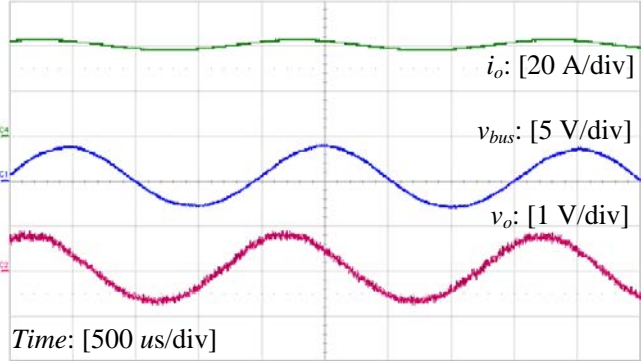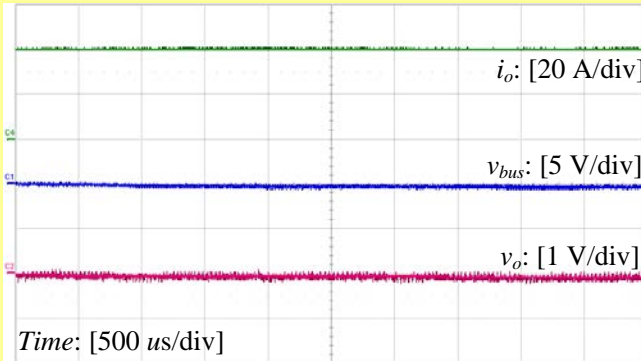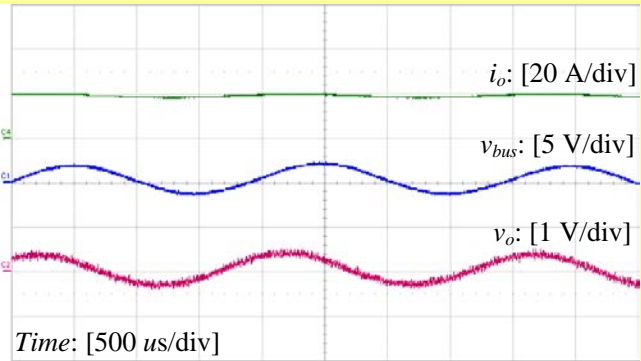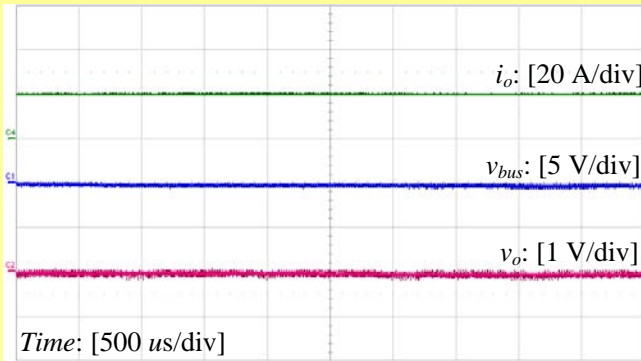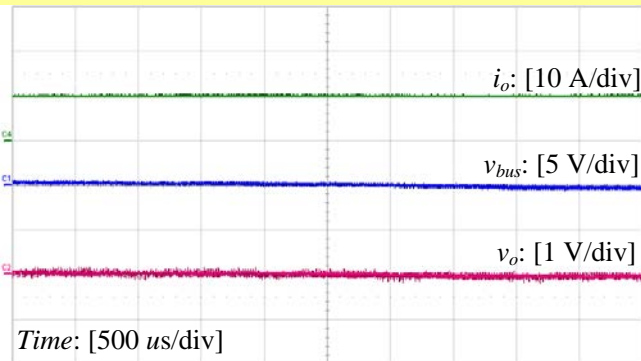
- At higher than 35% full-load,  $Z_{o_s}$  intersects with  $Z_{in\_L}$ . This means that the cascaded system is **unstable**.
- At lower than 35% full-load,  $Z_{o_s}$  does not intersect with  $Z_{in\_L}$ . This means that the cascaded system is **stable**.



	W/O Impedance Adaptor	With Impedance Adaptor
Full Load		
Half Load		
35% Full Load		<p><b>The impedance adaptor is not required to operate, and it is shut down.</b></p>

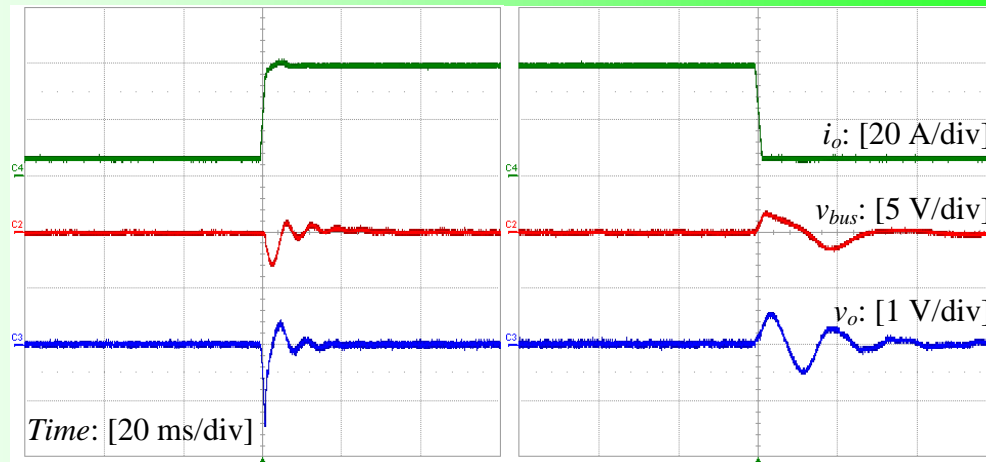

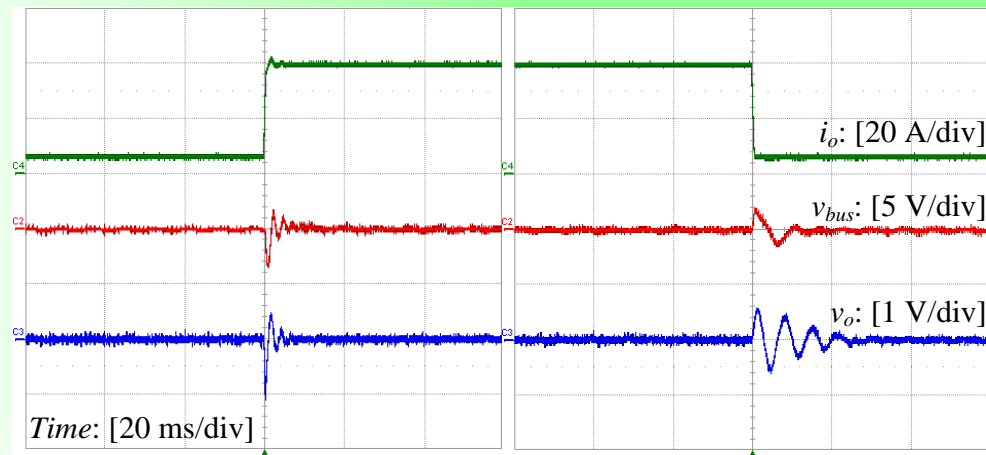With 1950  $\mu$ F Electrolytic capacitor



With the impedance adaptor



Fast  
dynamic  
response!

- Backgrounds
- General Impedance-Based Stability for Cascaded System
- Input Impedance Regulation for Load Converter
- Adaptive Impedance Adaptor
- **Conclusions**

- The concept of **bus voltage controlled converter (BVCC)** and **bus current controlled converter (BCCC)** is proposed, and any converter in the cascaded system can be classified as either a BVCC or a BCCC, thus a cascaded system can be represented in a general form regardless of its structure and operating mode.
- The **general impedance-based stability criterion** for cascaded system is proposed, and the equivalent loop gain is equal to the ratio of the shunt impedance of the **bus-side-port-impedances** of all the BVCCs and the **bus-side-port-impedances** of all the BCCCs.
- Regarding the load converter, which is a BCCC, **a method of regulating the input impedance based on virtual impedance** is proposed, which increases the **magnitude** or **phase** of the input impedance in the vicinity of the intersection frequency, thus ensuring the cascaded system stable.
- The **adaptive impedance adaptor** is proposed, which emulates a capacitor connected in parallel with the dc bus. This emulated capacitor **varies adaptively with the load**, and avoiding the impedance intersection over the full frequency range, ensuring the cascaded system stable. The adaptive impedance adaptor has the advantages of **fast dynamic response** compared with the passive capacitor and **modular design** without any information of the converters in the system.

This work is supported by the *National Nature Science Foundation of China* under Award 51277097.

Thank you very much for  
Your attention!